



Enrolment No. _____

HASMUKH GOSWAMI COLLEGE OF ENGINEERING, VAHELAL
MID SEMESTER EXAMINATION, SEPTEMBER-2016


Subject Code: 2130901
Subject Name: C&N
Time: 10:00 TO 10:50

Date: 26/09/2016
Sem: 3RD EE
Total Marks: 20

Instructions:

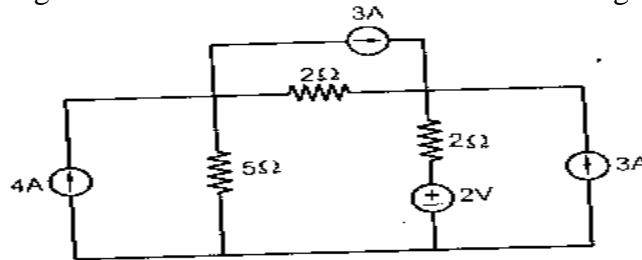
1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- QUE.1** (A) 1. What is time constant for RL circuit? 3
 2. Define Time Invariant Network
 3. Define Lumped Network
- (B) Explain source transformation to obtain voltage source from current source. 3
- QUE.2** (A) Draw the characteristics and differentiate between ideal current source and actual current source 3
- (B) Find currents through the 5 ohm resistors in the network of using mesh analysis 4




OR

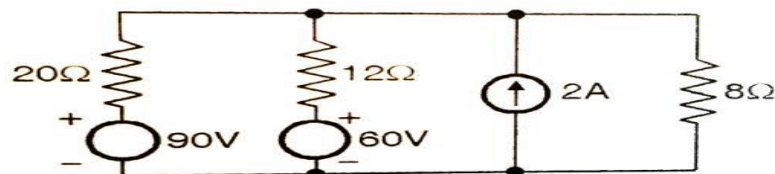- (B) Find current in 20 ohm resistance in the circuit shown in figure using superposition theorem 4



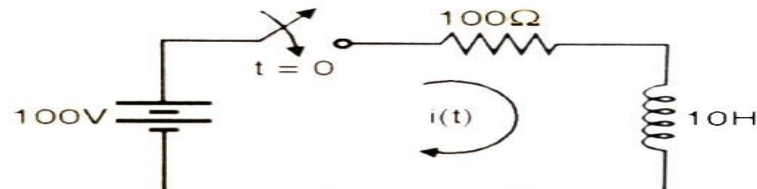- QUE.3** (A) In the circuit shown in figure, the switch 'K' is closed at $t=0$. Assuming no initial current through inductor. Find current at $t = 0.3$ sec 3



- (B) Drive the condition for maximum power transfer to the load for AC circuit 4

OR

- QUE.3** (A) Explain the procedure to obtain the transient response of a first order system. 3
- (B) State and Explain Norton's Theorem 4

***** ALL THE BEST *****